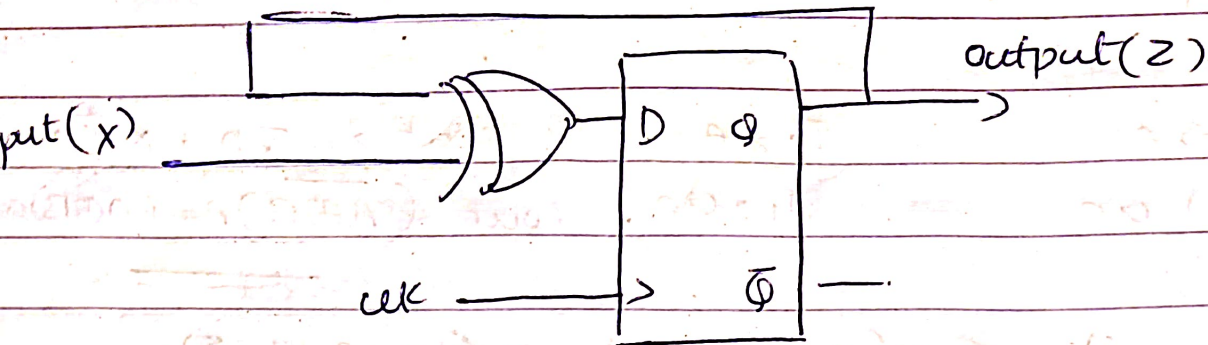


Assignment - Day 4 - Sequential

1) Explain the behaviour of the given circuit



XOR gate inputs are State Table

External input = x

Feedback input = Q

Present state (Q)

Input (x)

Q_{next}

$$D = x \oplus Q$$

0

0

0

$$Q_{next} = D$$

0

1

1

$$Q_{next} = x \oplus Q$$

1

0

1

$$Z_{next} = x \oplus Z$$

1

1

0

Case 1: $x = 0$

$$\Rightarrow Q_{next} = Q$$

Case 2: $x = 1$

$$\Rightarrow Q_{next} = \bar{Q}$$

The circuit behaves like a T flip flop

2. Design a posedge triggered D FF using 2:1 Muxes only

Master Latch $\Rightarrow M = \overline{clk} D + clk M$

Slave Latch $\Rightarrow Q = clk m + \overline{clk} Q$

$clk = 0$

Mux 1 input connection

I_0

D

I_1

m (feedback)

select

clk

Output

m

$clk = 1$

Mux 2 input connection

I_0

Q (feedback)

I_1


m

select

clk

Output

Q

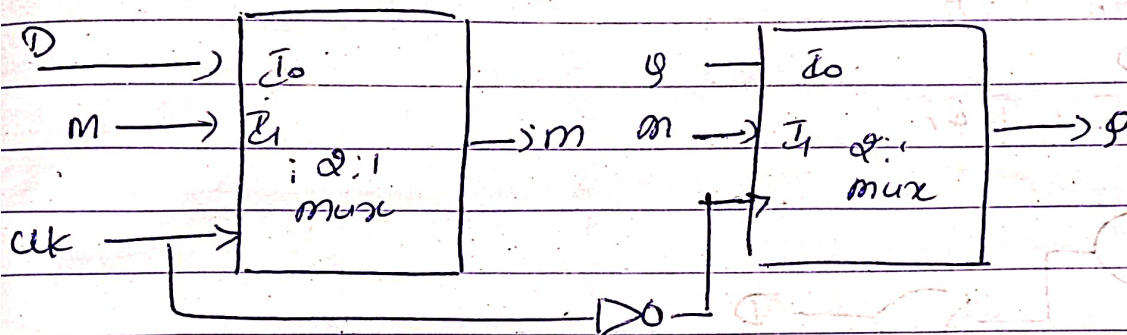

3. Design a negedge Triggered T-FF using 2:1 Muxes only

Characteristic equation of TFF is $Q_{next} = T \oplus Q$

For 2:1 Mux

select line - T

$I_0 = Q$

$I_1 = \overline{Q}$

$y = \overline{T}Q + T\overline{Q}$

$y = T \oplus Q$

Master latch $clk = 1$

Input connection

I_0

m (feedback)

I_1

$T \oplus m$

select

clk

Output

m

Slave latch, $clk = 0$

Input connection

I_0

m

I_1


Q (feedback)

select

clk

Output

Q

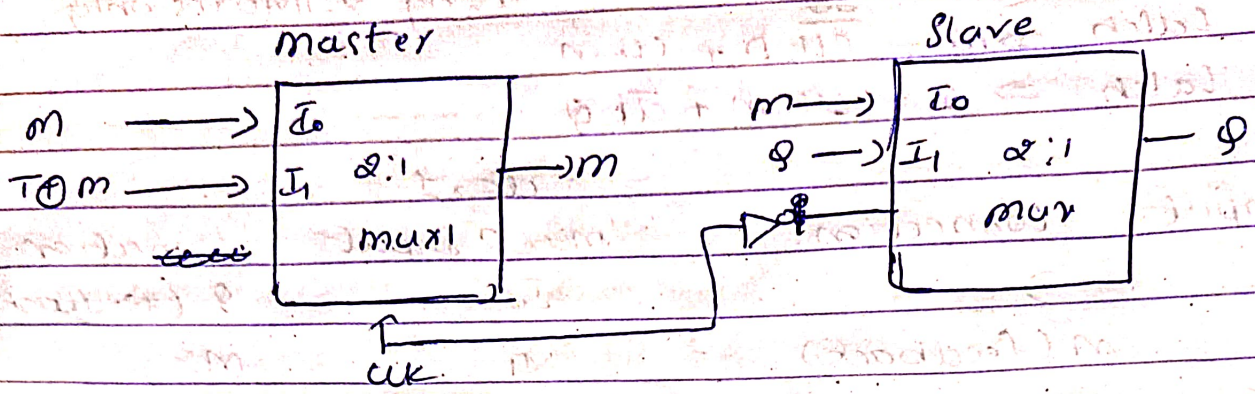


4) Convert by adding external gates:

a) A D Flip-flop to a JK flip-flop

$$Q_{n+1} = J\bar{Q}_n + \bar{K}Q_n$$

$$Q_{n+1} = D$$


$$D = J\bar{Q}_n + \bar{K}Q_n$$

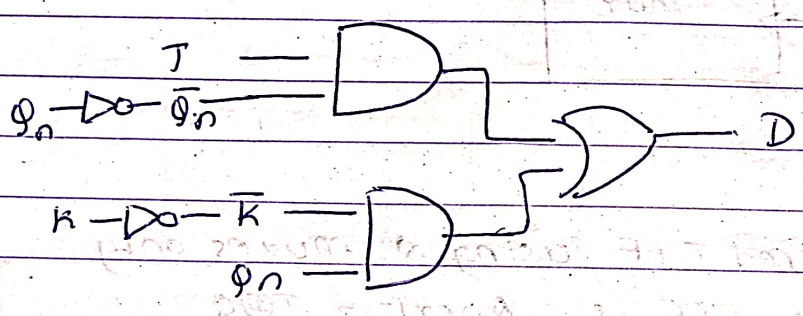

b) A T Flip-Flop to a D Flip flop


$$Q_{n+1} = T \oplus Q \quad Q_{n+1} = D \quad \Rightarrow \quad D = T \oplus Q$$

$$T = D \oplus Q$$

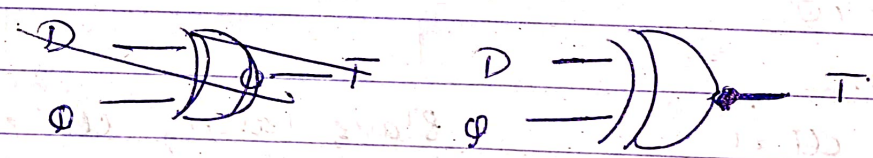

5. In a positive edge triggered JK flip flop, we have $J = Q'$ and $K = 1$ as shown in the figure below. Assume the flip flop was initially cleared and then worked for 6 clock pulses, find the sequence at the q output for

those 6 clock cycles

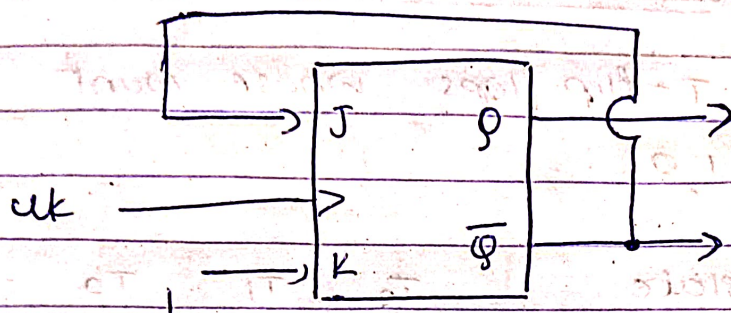

$$Q_{n+1} = J\bar{Q}_n + \bar{K}Q_n$$

$$K = 1 \Rightarrow \bar{K} = 0 \quad J = \bar{Q}$$

$$Q_{n+1} = \bar{Q} \cdot \bar{Q} + 0$$

$$Q_{n+1} = \bar{Q} \quad (\text{Toggles on every clock pulse})$$

Clock pulse	present Q	$J = Q'$	K	next Q
0	0	1	1	1
1	1	0	1	0
2	0	1	1	1
3	1	0	1	0
4	0	1	1	1
5	1	0	1	0
6	0	1	1	1

Sequence is $0 \rightarrow 1 \rightarrow 0 \rightarrow 1 \rightarrow 0 \rightarrow 1 \rightarrow 0$